

Simulation : NMOS

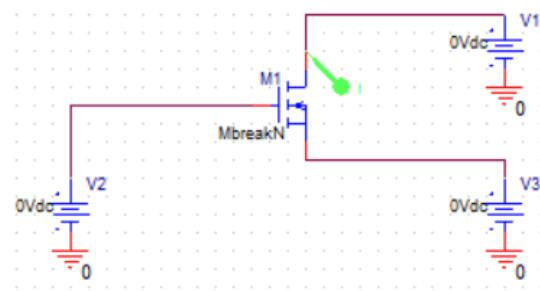


Figure : Circuit Diagram for NMOS.

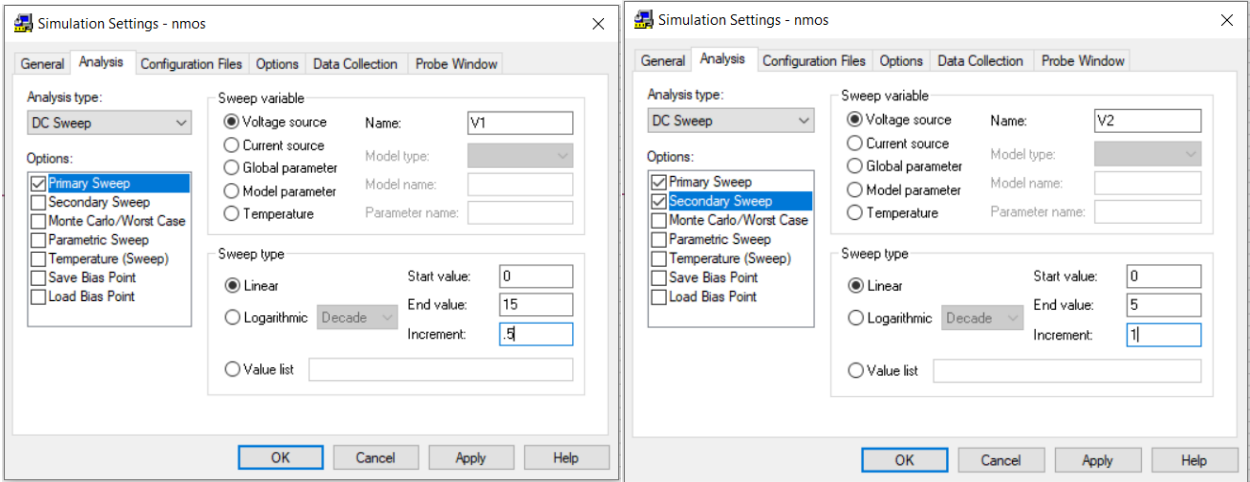


Figure : Input for NMOS.

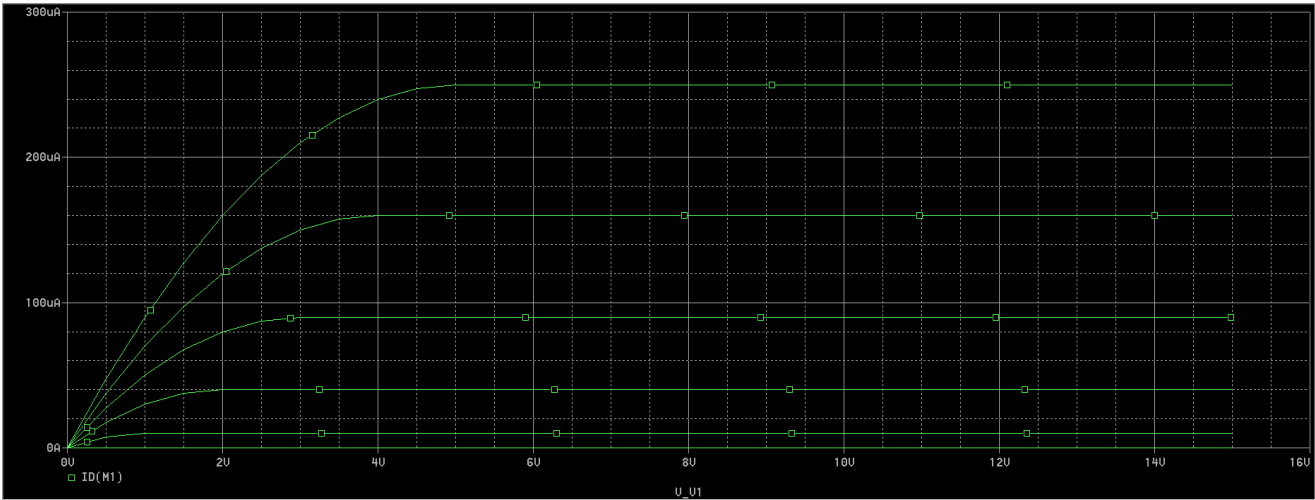


Figure : Resultant Curve for NMOS.

Simulation : PMOS

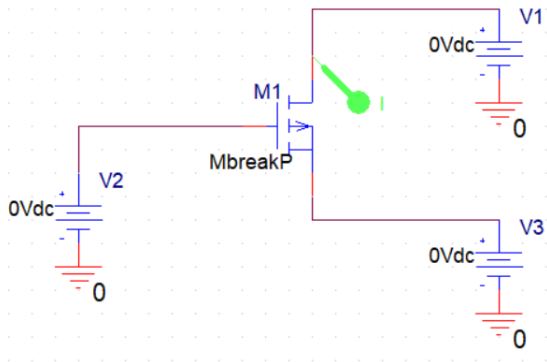


Figure : Circuit Diagram for PMOS.

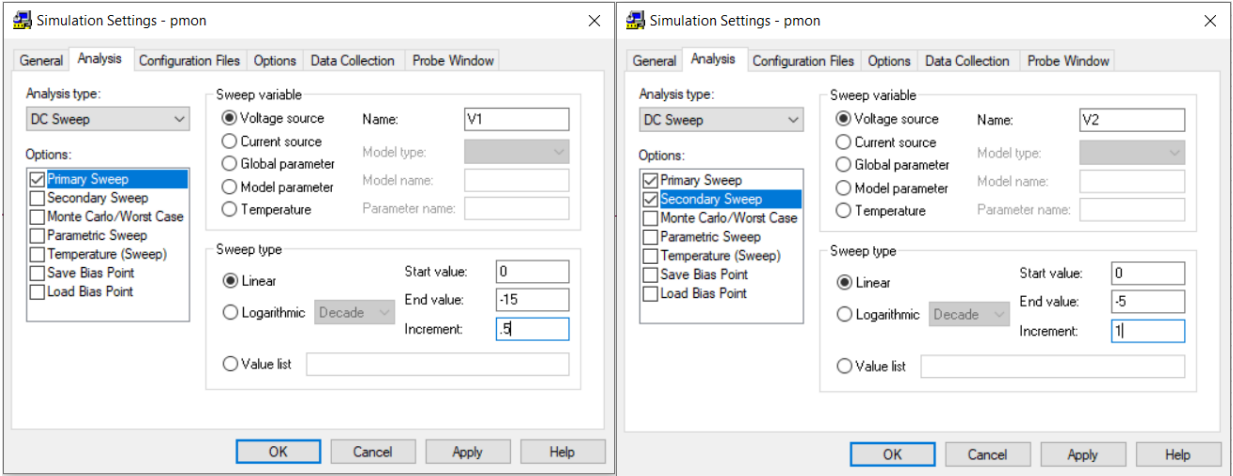


Figure : Input for PMOS.

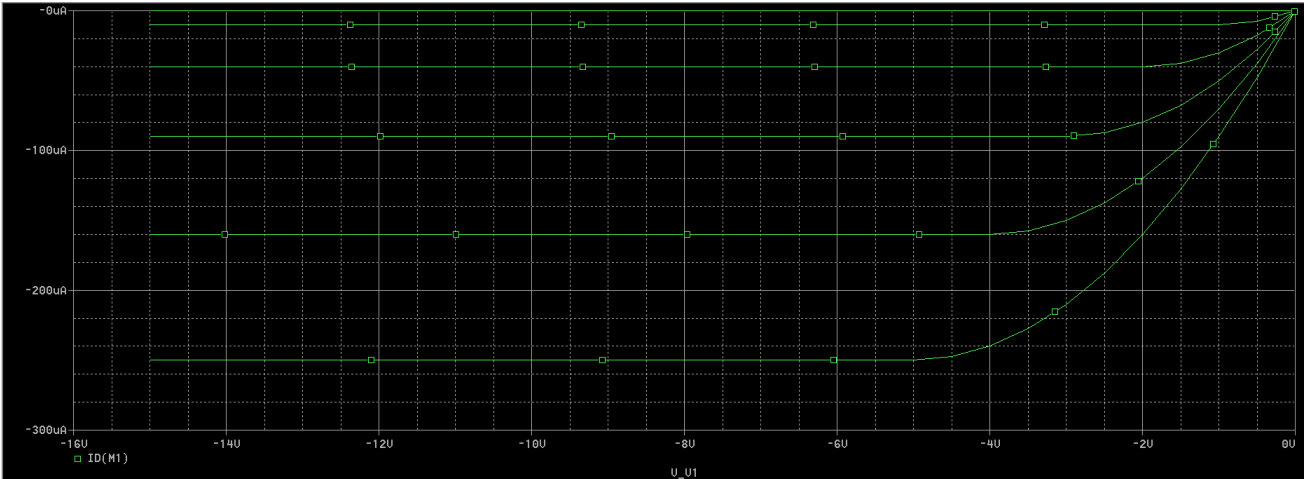


Figure : Resultant Curve for PMOS.