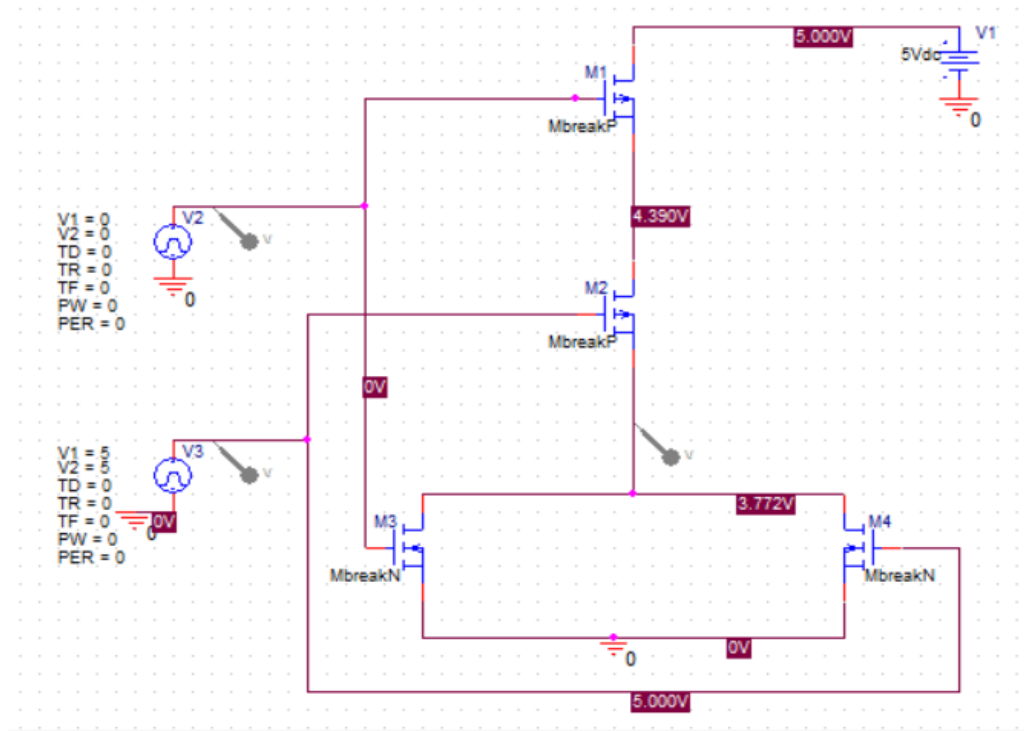



Simulation Profile : 1

### Circuit Diagram :



**Figure : Circuit Diagram.**

### Simulation Outcome :

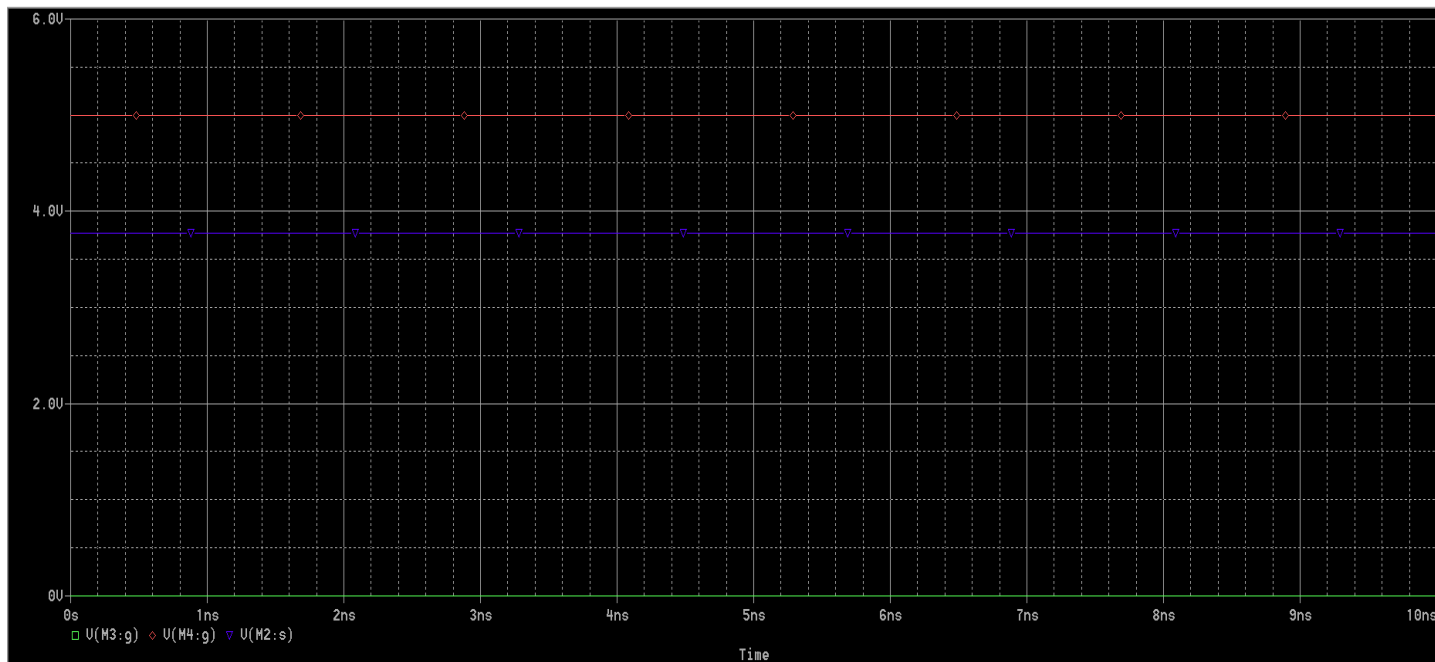

**Figure :** Simulation outcome.

Simulation Profile : 2

Circuit Diagram :

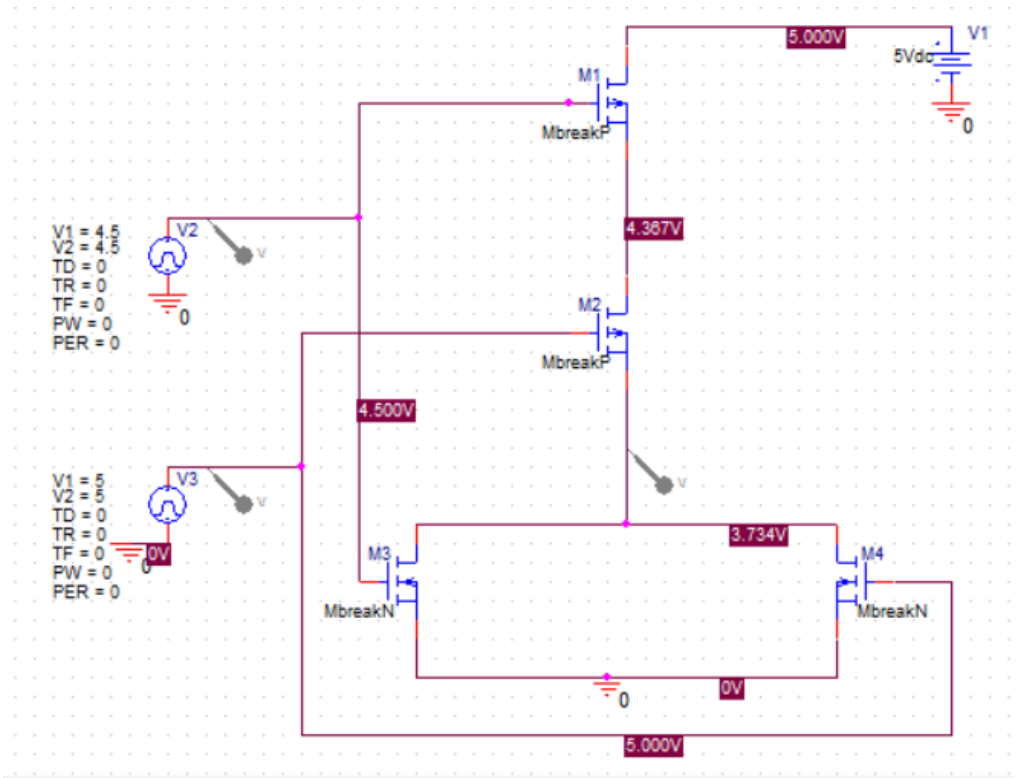


Figure : Circuit Diagram.

Simulation Outcome :

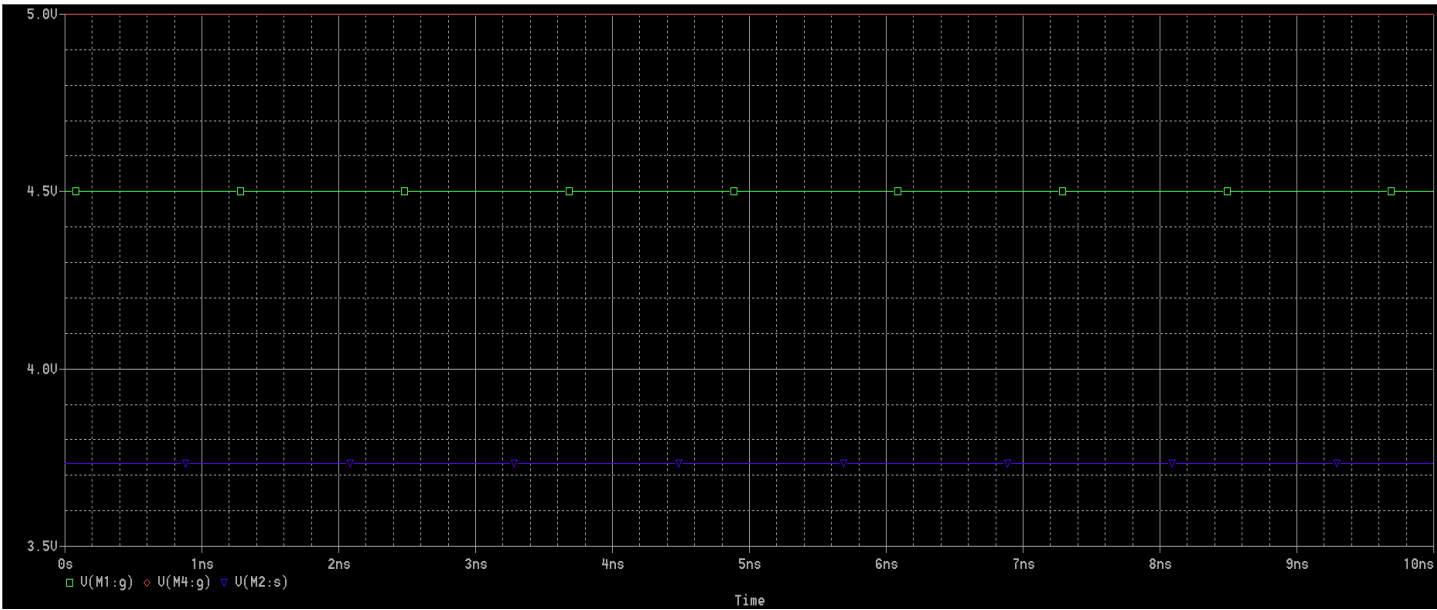


Figure : Simulation outcome.

## NOR Gate :

a)




*NOR Gate*

b)

A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	0

*NOR accuracy table*

## Simulation :

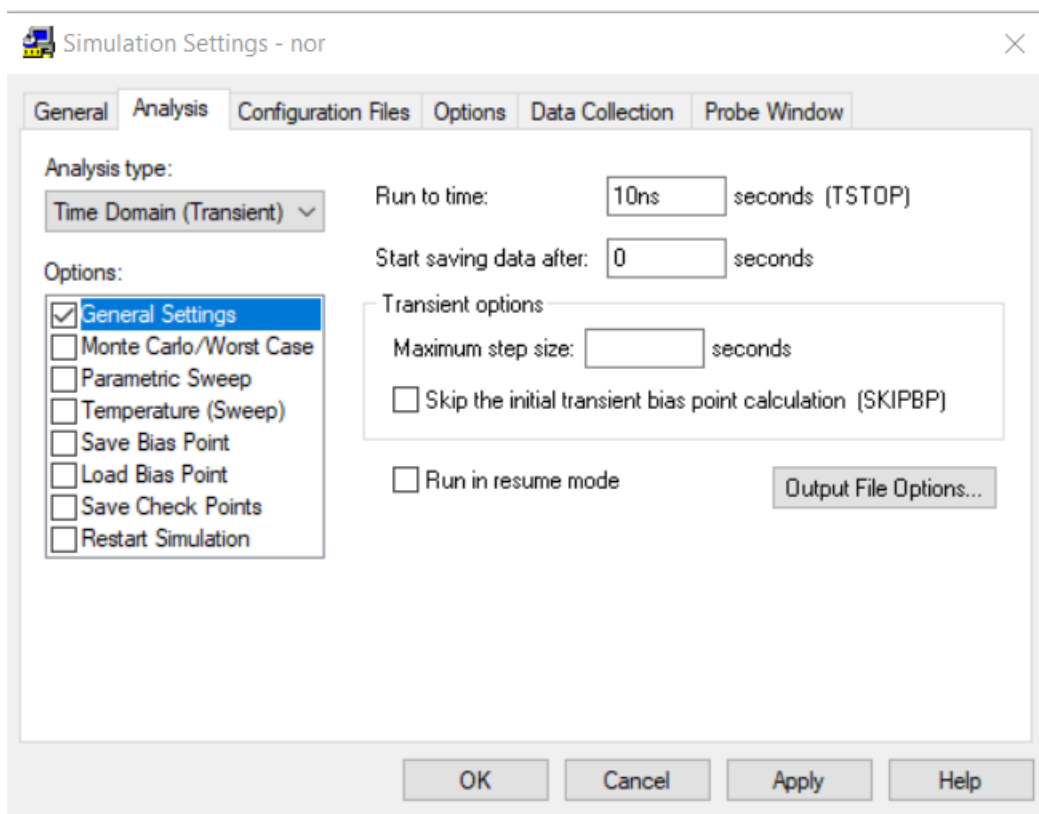

**Figure :** Simulation profile setting.